

CHAITANYA BHARATHI INSTITUTE OF TECHNOLOGY (Autonomous)**B.E. III Sem (Main) Examination February/March 2022****Basic Electronics****(Common to CSE, CSE-AI&ML, CSE-IoT&CS)****Time: 3 Hours****Max Marks: 60****Note:** Answer **ALL** questions from **Part-A & Part –B (Internal Choice)** at one place in the same order**Part - A**
(5Q X 3M = 15 Marks)

	M	CO	BT
1 Differentiate diffusion and drift currents in PN-Junction semiconductor	(3)	1	2
2 Illustrate h-parameter equivalent circuit for CE-Configuration.	(3)	2	2
3 List out the advantages of Negative Feedback Amplifier.	(3)	3	1
4 What are the ideal characteristics of an OPAMP?	(3)	4	1
5 Define the principle of photo diode.	(3)	5	1

Part – B
(5Q X 9M = 45 Marks)

	M	CO	BT
6 (a) Illustrate the energy levels and band gap of Intrinsic and Extrinsic Semiconductor.	(5)	1	2
(b) Analyze the characteristics of P-N Junction diode.	(4)	1	4
(OR)			
7 (a) Determine the Full wave Bridge Rectifier's Ripple factor and efficiency.	(5)	1	4
(b) Analyze the role of filters in rectifiers.	(4)	1	4
8 (a) Explain how Zener diode acts as a voltage regulator.	(5)	2	4
(b) Interpret the Avalanche and Zener Breakdown mechanisms.	(4)	2	4
(OR)			
9 (a) Derive the Common Source JFET parameters.	(5)	2	2
(b) Distinguish BJT and FET in various parameters.	(4)	2	4
10 (a) Derive the expression for frequency of Colpitts oscillator with necessary illustrations.	(5)	3	4
(b) Distinguish positive and negative feedback amplifiers.	(4)	3	4
(OR)			
11 (a) Evaluate the frequency of RC-phase shift oscillator with necessary illustrations.	(5)	3	2
(b) What are the necessary conditions to get the sustained oscillations?	(4)	3	1
12 (a) Determine the efficiency of Class B amplifier.	(5)	4	3
(b) Compare Class A, Class AB and Class C power amplifiers.	(4)	4	4

(OR)

- 13 (a) Derive the expression for integrator and differentiator using operational amplifier. (5) 4 4
(b) Write down the ideal characteristics of OP-AMP. (4) 4 4
- 14 (a) Explain about the characteristics of SCR. (5) 5 4
(b) Analyze the working of Strain gauge and specify its applications. (4) 5 4
- (OR)**
- 15 (a) Explain the working of LCD and specify its construction details. (5) 5 4
(b) Give the constructional details of CRO. (4) 5 1
